


- Guidelines:-
- Answer all 5 questions.
  - Make necessary assumptions, with justifications.
  - Attempt all parts of a question in one place. Box/Encircle the final answer.

Q-1. If the Laplace Transform of  $f(t)$  is  $F(s)$ .

- Derive the Laplace transform of  $\{t f(\alpha t)\}$  in terms of  $F(s)$ . Note ' $\alpha$ ' is a constant related to scaling. [5]
- Derive the Laplace Tx. of  $\{t^{-1} f(t)\}$  in terms of  $F(s)$ . Using the above result, evaluate the integral,  $\int_0^{\infty} \frac{\sin t}{t} e^{-t} dt$ . [10]

Q-2. Consider the signal,  $f(t) = \frac{1}{\sqrt{t}} u(t)$ , where  $u(t)$  is the unit step function. We define  $g(t) \triangleq f(t) * f(t)$ , where '\*' is the convolution operator. Using the result of  $g(t)$ , derive the Laplace Tx. of  $f(t)$ . [15]  
[Hint:-  $\frac{d(\sin^{-1}x)}{dx} = \frac{1}{\sqrt{1-x^2}}$ ]

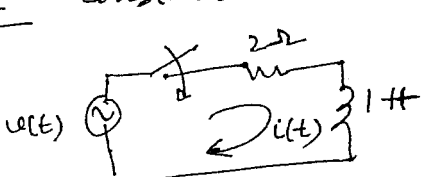Q-3. Consider the R-L ckt. [Note:- You cannot use Laplace Tx.]




- Write down the Differential Eq<sup>n</sup>. relating  $i(t)$  &  $v(t)$ . [5]
- Find the sol<sup>n</sup>. to the homogeneous Eq<sup>n</sup>. [5]

(c) If  $v(t) = e^{-2t} (1 + t^2 \sin \omega t)$ . Find the particular sol<sup>n</sup>. [10]

Q-4 System design problem:-

Consider the following ckt:-

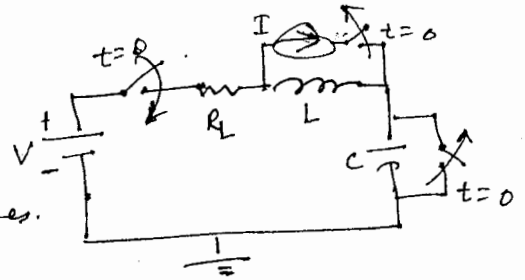

→  $V$  &  $I$  are DC voltage & current sources.

→ Load resistance,  $R_L = 25 \Omega$


→ Capacitor =  $50 \text{ pF}$ .

→ Inductor =  $10 \text{ nH}$ , with a Quality factor of  $2\sqrt{2}$ , at the resonant frequency of the L-C tank network.

- Write down the integro-differential eqn, that  $i(t)$  satisfies for  $t \geq 0$ . [Note: that the inductor is not ideal]. [5]
- Find the soln. to the Differential Eqn. along with initial conditions. [5]
- Consider that  $i(t)$  reaches a peak at  $t = (2 \ln 2) \text{ ns}$ . Sketch the waveform by finding the appropriate value of  $V$  &  $I$ . Find the pulse repetition frequency (PRF)\*. [12.5]
- Consider now that  $i(t)$  reaches a peak at  $t = (2 \ln 2) \text{ ns}$ . Sketch the corresponding waveform & find the PRF.\* [12.5]

\* NOTE:- PRF is related to inverse of minimum time period. The minimum time period consists of the time reqd. for the pulse to decay to 5% of its peak value and the charging time (of the current through the inductor to the appropriate initial value).

Q-5

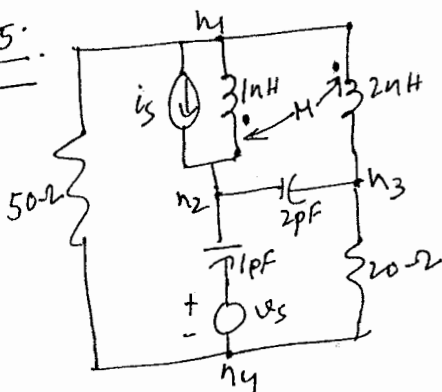

$n_1, n_2, n_3, n_4$  are the nodes.

Mutual inductance =  $0.5 \text{ nH}$ .

Freq =  $100 \text{ MHz}$ ,  $v_s = 0.25 \sin \omega t$

$i_s = 0.3 \cos \omega t$

a) Write down the ~~Admittance~~ Incidence Matrix, Fundamental loop matrix & Impedance matrix. [5]

b) Derive the matrix formulation of the loop currents and the corresponding matrix elements. [10]