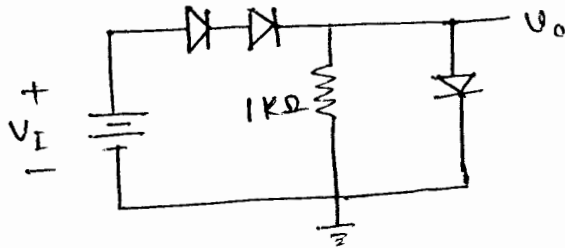



Date: 02/02/2011 FN/AN Time: 2/3 Hrs. Full Marks: 60 No. of Students: 600
 Autumn / Spring Semester, Deptt: E & ECE Sub. No: EC 21101
 2nd Yr. B.Tech. (H) / B.Arch. (H) / M.Sc. Sub. Name: _____
 Instruction: _____

1.
 a) The reverse-saturation current of each diode in the circuit shown in figure is $I_s = 2 \times 10^{-13}$ A. Determine the input voltage V_I required to produce an output voltage of $V_o = 0.60$ V. 6



- b) A pn junction diode is in series with a 100-kΩ resistor and a 3.5 V power supply. The reverse saturation current of the diode is $I_s = 5$ nA. Determine the diode current and voltage if the diode is forward bias and reverse bias. 6

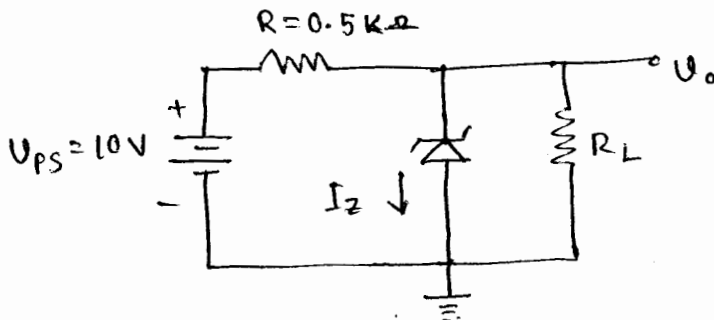2.
 a) Consider the zener diode circuit shown in figure. The zener breakdown voltage is $V_z = 5.6$ V at $I_z = 0.1$ mA and the incremental zener resistance is $r_z = 10$ Ω. Determine V_o with no load ($R_L = \infty$) and find the change in output voltage if $V_{ps} = 10$ V and $R_L = 2$ kΩ. 7




- b) A voltage regulator consists of a 6.8 V zener diode in series with a 200 Ω resistor and a 9 V power supply. Neglect r_z . Determine the diode current and power dissipation. 5

3.
 a) The reverse-saturation current of a silicon pn junction diode at 300 K is $I_s = 10^{-12}$ A. Determine the temperature range over which I_s varies from 0.5 pA to 50 pA. 6
 b) A pn junction diode has saturation current $I_s = 10^{-15}$ A. Determine the diode voltage if $I_D = 150$ μA. Also determine the diode current for $V_D = 0.2$ V, 0 V and -3 V. 6

4.

a) Sketch V_o vs time for the circuit given in figure. Assume that $V_\gamma = 0$ V.


6

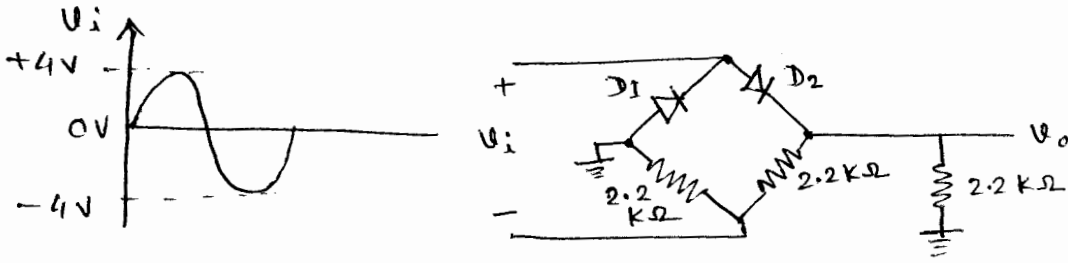

b) For the circuit in figure show that for $v_1 > 0$, output voltage is given by

4

$$v_o = v_1 - V_T \ln(v_o / I_s R)$$

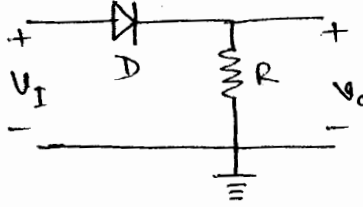


c) Mention advantages of bridge rectifier over conventional full-wave rectifier.

2


5.

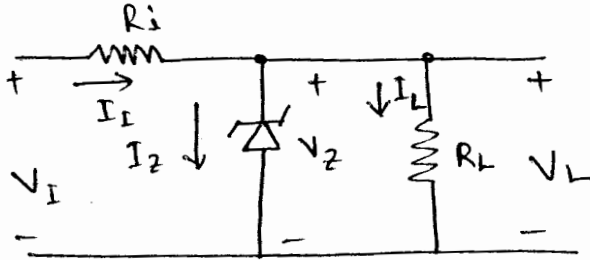a) In the voltage regulator circuit in Figure, let $V_1 = 6.3$ V, $R_i = 12 \Omega$ and $V_z = 4.8$ V. The zener diode current is to be limited to the range $5 < I_z < 100$ mA. Determine the range of possible load currents and load resistances. Also determine the power rating required for the zener diode and load resistor.



b) If the diode cut-in voltage is 0.7 V, then determine the out-put voltage (V_o) for the following circuits.

6

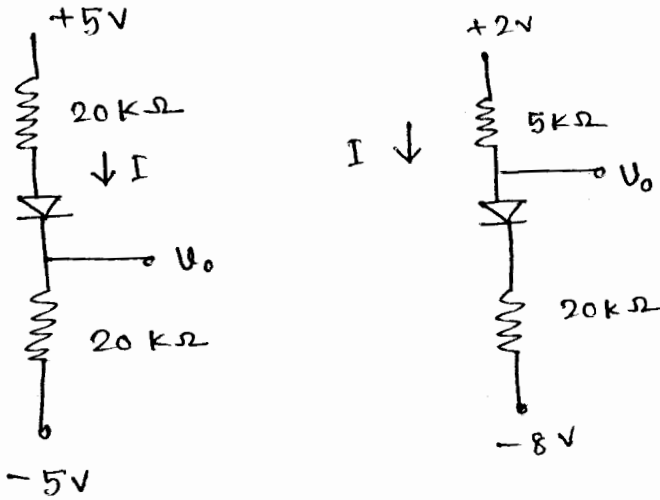

Avogadro's number	$N_A = 6.02 \times 10^{23}$ molecules/mole
Boltzmann's constant	$k = 1.38 \times 10^{-23}$ J/K $= 8.62 \times 10^{-5}$ eV/K
Electronic charge (magnitude)	$q = 1.60 \times 10^{-19}$ C
Electronic rest mass	$m_0 = 9.11 \times 10^{-31}$ kg
Permittivity of free space	$\epsilon_0 = 8.85 \times 10^{-14}$ F/cm $= 8.85 \times 10^{-12}$ F/m
Planck's constant	$h = 6.63 \times 10^{-34}$ J-s $= 4.14 \times 10^{-15}$ eV-s
Room temperature value of kT	$kT = 0.0259$ eV
Speed of light	$c = 2.998 \times 10^{10}$ cm/s

Prefixes:

1 Å (angstrom) = 10^{-8} cm	milli-, m- = 10^{-3}
1 μm (micron) = 10^{-4} cm	micro-, μ- = 10^{-6}
1 nm = 10 Å = 10^{-7} cm	nano-, n- = 10^{-9}
2.54 cm = 1 in.	pico-, p- = 10^{-12}
1 eV = 1.6×10^{-19} J	kilo-, k- = 10^3
	mega-, M- = 10^6
	giga-, G- = 10^9

A wavelength λ of 1 μm corresponds to a photon energy of 1.24 eV.

		E_g (eV)	μ_n (cm ² /V-s)	μ_p (cm ² /V-s)	m_n^*/m_0 (m_n, m_l)	m_p^*/m_0 (m_h, m_v)	a (Å)	ϵ_r	Density (g/cm ³)	Melting point (°C)
Si	(i/D)	1.11	1350	480	0.98, 0.19	0.16, 0.49	5.43	11.8	2.33	1415
Ge	(i/D)	0.67	3900	1900	1.64, 0.082	0.04, 0.28	5.65	16	5.32	936
SiC (α)	(i/M)	2.86	500	—	0.6	1.0	3.08	10.2	3.21	2830
AlP	(i/Z)	2.45	80	—	—	0.2, 0.63	5.46	9.8	2.40	2000
AlAs	(i/Z)	2.16	1200	420	2.0	0.15, 0.76	5.66	10.9	3.60	1740
AlSb	(i/Z)	1.6	200	300	0.12	0.98	6.14	11	4.26	1080
GaP	(i/Z)	2.26	300	150	1.12, 0.22	0.14, 0.79	5.45	11.1	4.13	1467
GaAs	(d/Z)	1.43	8500	400	0.067	0.074, 0.50	5.65	13.2	5.31	1238