

R

DEPARTMENT OF ELECTRICAL ENGINEERING, IIT KHARAGPUR
 END-SEMESTER EXAMINATION (Autumn 2009-10)
 SUBJECT: SIGNALS & NETWORKS (EE21101)

Date: 25 November 2009

Time: 2 P.M. --- 5 P.M.

Full Marks: 100

Instructions:

- (1) This question paper consists of SIX questions. Answer any FIVE questions.
- (2) The symbols express their standard meanings as used for this subject.
- (3) Make appropriate assumptions wherever necessary (with justifications).

QUESTION 1

- (A) For the network shown in Fig. Q1A, the switch is in position 'a' for a long time and then is moved to position 'b' instantaneously at time $t = 0$. Determine the current $y(t)$ for $t > 0$ using s-domain equivalent circuit analysis. [10 marks]

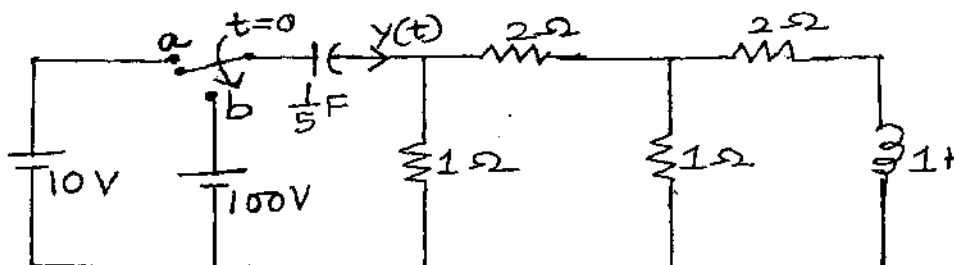


Fig. Q1A

- (B) Using time-domain approach, find the unit impulse response of an LTI system specified by the differential equation $\{x(t) = \text{input and } y(t) = \text{output}\}$

$$\frac{d^2 y(t)}{dt^2} + 6 \frac{dy(t)}{dt} + 9y(t) = 2 \frac{dx(t)}{dt} + 9x(t) \quad [4 \text{ marks}]$$

- (C) An LTI system is described by the differential equation $\{x(t) = \text{input and } y(t) = \text{output}\}$

$$\frac{d^2 y(t)}{dt^2} + 4 \frac{dy(t)}{dt} + 4y(t) = \frac{dx(t)}{dt} + x(t)$$

If $y(0^-) = 2$, $\dot{y}(0^-) = 1$ and $x(t) = e^{-t}u(t)$ $\{u(t)$ is the unit-step signal $\}$, solve the differential equation using Laplace transform to find $y(t)$. Determine the zero-input and zero-state components of the solution. [6 marks]

QUESTION 2

- (A) For the network shown in Fig. Q2A, determine the voltage transfer ratio V_2/V_1 and the input impedance at port 1 if $Z_a Z_b = R_0^2$. [6 marks].

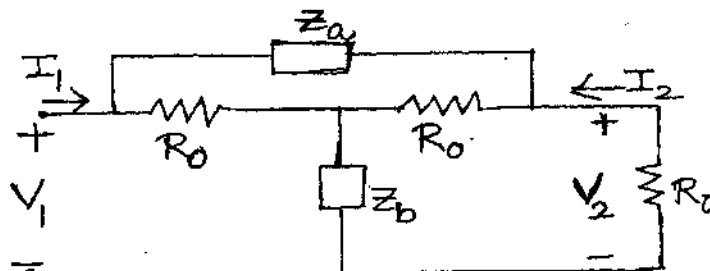


Fig. Q2A

(B) Sketch the asymptotic Bode plot of the following network function.

$$G(s) = \frac{10^4(s+40)}{s^2 + 410s + 4000}$$

Determine the value of $G(j800)$ from the Bode plot.

[8 marks]

(C) In the network shown in Fig. Q2C, all initial conditions are zero. Determine the equivalent Thevenin network at the terminals $a-b$. $v_1(t) = u(t)$, where $u(t)$ is the unit-step signal.

[6 marks]

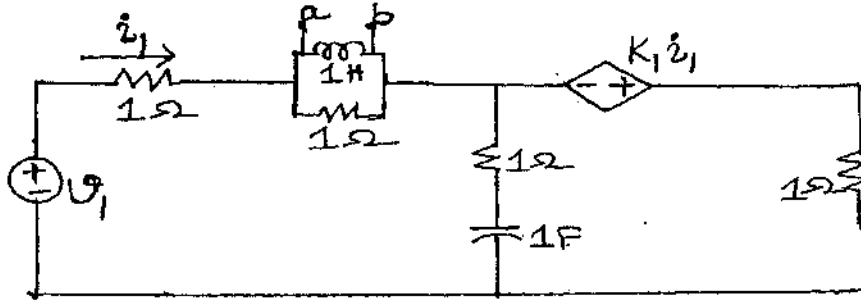


Fig. Q2C

QUESTION 3

(A) Determine the y -parameters of the two-port network shown in Fig. Q3A.

[8 marks]

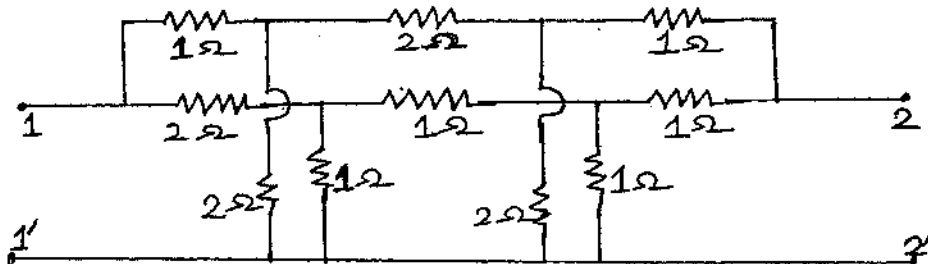


Fig. Q3A

(B) Derive a set of normal state equations for the circuit shown in Fig. Q3B. $v_s = 5 \sin 2t u(t)$, where $u(t)$ is the unit-step signal.

[6 marks]


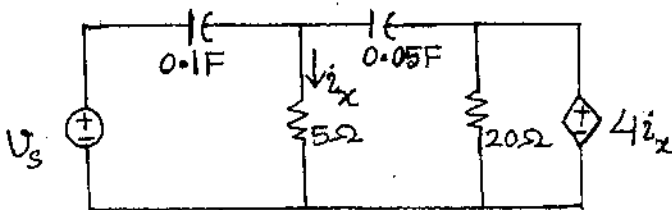


Fig. Q3B

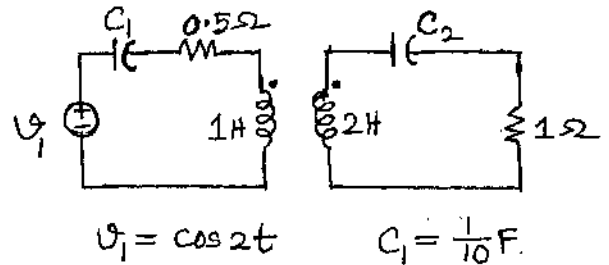

$$v_1 = \cos 2t$$

$$C_1 = \frac{1}{10} \text{ F}$$

Fig. Q3C

(C) For the network shown in Fig. Q3C, what value of C_2 will result in maximum power delivery to the 1Ω resistor load?

[6 marks]

QUESTION 4

- (A) Use modified nodal analysis to derive the matrix equation that can be used to determine the node voltages V_a , V_b and V_c in the circuit shown in Fig. Q4A.

[5 marks]

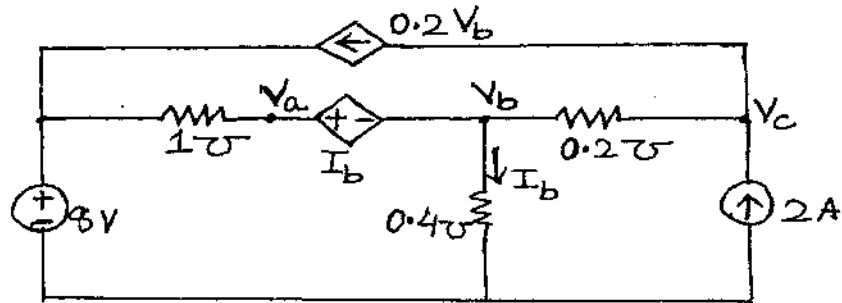


Fig. Q4A

- (B) Derive the matrix equation using graph-theoretic nodal analysis of the network shown in Fig. Q4B and use it to determine all the branch voltages.

[8 marks]

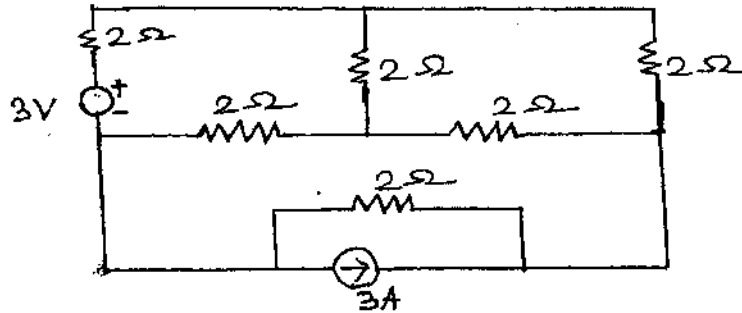


Fig. Q4B

- (C) Derive the conditions for which the two networks shown in Fig. Q4C-1 and Fig. Q4C-2 have identical y - or z -parameters.

[7 marks]

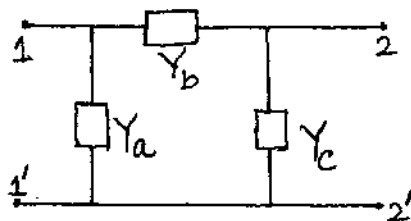


Fig. Q4C-1

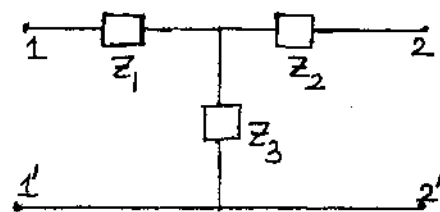


Fig. Q4C-2

QUESTION 5

- (A) An LTI continuous-time system has unit impulse response, $h(t)$, given by

$$h(t) = u(t) - u(t - 1), \text{ where } u(t) \text{ is the unit-step signal.}$$

- Which type of filter most accurately describes the behavior of this system?
- What are the poles/zeros of this filter? Explain your answer.
- Can you find the impulse response of the inverse system of this filter? If so, provide it.

[8 marks]

(B) Determine the transfer function of a fourth order Butterworth lowpass filter. Use this to find the transfer function of a corresponding bandpass filter with midband frequency of 1 rad/sec and bandwidth of 0.1 rad/sec.

[8 marks]

(C) A student suggests a possible lowpass-to-highpass filter transformation given by:

$$H_{hp}(s) = 1 - H_{lp}(s),$$

where $H_{lp}(s)$ is the transfer function of an ideal lowpass filter and $H_{hp}(s)$ is the transfer function of an ideal high pass filter. In general, will this transformation work? Explain.

[4 marks]

QUESTION 6

(A) Determine the amplitude and phase spectra for the currents i_1 and i_2 for the network shown in Fig. Q6A-1 when excited by the current source forcing function as shown in Fig. Q6A-2.

[8 marks]

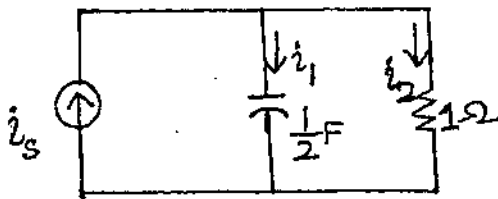


Fig. Q6A-1

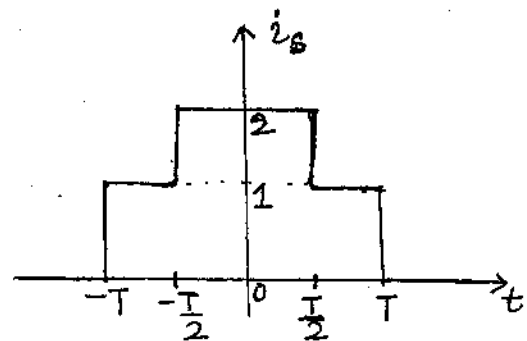


Fig. Q6A-2

(B) The signal $x(t)$, shown in Fig. Q6B, is approximated by the first $2N+1$ terms (from $n = -N$ to N) in its exponential Fourier series. Determine the value of N if this $(2N+1)$ -term Fourier series power is to be no less than 99.75% of the power of $x(t)$.

[6 marks]

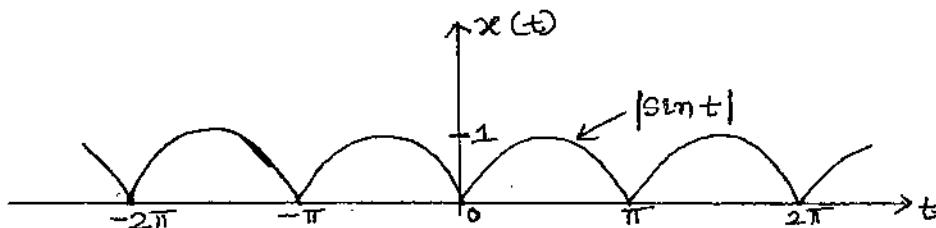


Fig. Q6B

(C) The following information about a discrete-time periodic signal $x[n]$ with a period of 8 and Fourier coefficients a_k is given:

(i) $a_k = -a_{k-4}$

(ii) $x[2n+1] = (-1)^n$

Sketch one period of $x[n]$.

[6 marks]