 


INSTRUCTIONS

1. All waveform sketches / diagrams must be neatly drawn and clearly labeled.
2. The final answers (numerical values with unit) must be underlined or enclosed in a box.
3. For any value related to any device parameter or circuit parameter, which you may find not given with a problem, assume suitable value for such parameter.
4. Answers must be brief and to the point. Partial credit will be awarded for correct attempt.
5. Start working out the solution for every problem in a new page.
6. For each problem, please write the answers of all its parts together and avoid writing answers of its various parts at different locations in your answer-script.

1. Problem on MOS Circuits: 20 points




(1a) Refer to the circuit shown in Figure 1.

$V_{Tn} = 1 \text{ V}$ ,  $\mu_n C_{OX} = 100 \text{ uA/V}^2$ ,  $\lambda_n = 0 \text{ V}^{-1}$   
 $W/L = 2 \text{ um} / 1\text{um}$ ,  $V_{DD} = 5 \text{ V}$ ,  $R_D = 10\text{K ohm}$

Draw the output waveform for the following conditions:  
 (In each case show the max. and min. values of  $V_{out}$ )

- $V_{in} = 2 + 0.1 \sin(2\pi \cdot 10^3 \cdot t) \text{ V}$  [4]
- $V_{in} = 5 + 0.1 \sin(2\pi \cdot 10^3 \cdot t) \text{ V}$  [4]

Figure 1. NMOS driver with resistor load

 

(1b) Refer to the circuit shown in Figure 2.

$V_{Tn} = 1 \text{ V}$ ,  $\mu_n C_{OX} = 100 \text{ uA/V}^2$ ,  $\lambda_n = 0 \text{ V}^{-1}$ ,  
 $W/L = 2 \text{ um} / 1\text{um}$ ,  $R_S = 10\text{K ohm}$

When input voltage  $V_X$  varies from 0V to 5V, plot the following:

- Source voltage  $V_S$  vs. input  $V_X$  [4]
- Drain current  $I_X$  vs. input  $V_X$  [4]
- Small signal resistance,  $r (= \Delta V_X / \Delta I_X)$  vs. input  $V_X$  [4]

Figure 2. NMOS circuit

2. Problem on OPAMP circuit: 10 points

 


Figure 3. OPAMP circuit for (2a)

(2a) For the circuit in Figure 3, assume ideal OPAMP.

- For  $n > 1$ , find the voltage gain,  $v_o / v_{in}$ . [5]
- For  $n < 1$ , comment on how the circuit will behave. [1]

 


Figure 4. OPAMP Circuit for (2b)

(2b) For the circuit shown in Figure 4, assume ideal OPAMP.

- Express  $v_o$  in terms of  $v_1$  and  $v_2$ . [4]

3. Problem on OPAMP and Feedback circuits: 10 points

 


Figure 5. OPAMP Circuit for (3a)

(3a) Refer to the circuit shown in Figure 5. Each of the switches  $S_1$ ,  $S_2$  and  $S_3$  can be either in position-1 (GND) or in position-2 (-5V).

- For all possible switch-position combinations, determine  $V_o$ . [5]

 


Figure 6. BJT Circuit for (3b)

(3b) Refer to the circuit shown in Figure 6. The output is taken as the voltage  $v_o$  while the potential difference across  $R_E (= v_E)$  is used as the negative feedback signal. Ignore Early effect.

- Identify the nature of the feedback. [1]
- Find the expression for small-signal voltage gain,  $v_o/v_{in}$ . [2]
- Find the expression for small-signal input impedance,  $R_{in}$ . [1]
- Find the expression for small-signal output impedance,  $R_o$ . [1]

4. Problem on logic circuits: 10 points

 


Figure 7. 1-bit Subtractor

(4a) Design the logic circuit using gates for the block shown in Figure 7, which subtracts the bit Y from bit X and outputs the difference bit D and a borrow bit B. [5]

(4b) Suitably cascade more than one blocks of Figure 7 to design a two bit subtractor which will subtract  $\{Y_1, Y_0\}$  from  $\{X_1, X_0\}$ . [5]

5. Problem on logic circuits: 10 points

(5a) Simplify the logic circuit in Figure 8 using Karnaugh Map. [5]

 


Figure 8. Logic Circuit for (5a)

(5b) For the circuit in Figure 9, sketch the Q output vs. time, with reference to the inputs A and B shown in Figure 10. Assume that the flip-flop is initially cleared. [5]

 


Figure 9. Logic Circuit for (5b)

 


Figure 10. Input waveforms of A and B for (5b)