



INDIAN INSTITUTE OF TECHNOLOGY, KHARAGPUR

Date.....FN/AN Time: 3 Hrs Full Marks: 100 No. of Students: 177
Autumn Semester Deptt.: E & ECE Sub. No. : EC21101
2nd year B.Tech (H)/ M.Sc. Sub. Name: Basic Electronics


Note: Attempt all the questions.

Answer to all the parts of a question should be attempted in the sequence and at one place only.


- Q.1 (a) What is the value of the current and junction potential in a short circuited p-n junction diode and why? 2
(b) What is Pauli's exclusion principle. 2
(c) What is the difference between electron hole recombination in a semiconductor bar and collision between an electron and positron in free space? 2
(d) What happens to holes at an Ohmic contact between semiconductor bar and external circuit? 2
(e) Why the mobility of an electron is typically higher than that of a hole in a particular intrinsic semiconductor at a particular temperature? 2
(f) In a simple circuit between two points A and B lies a diode and a resistance of value R Ohm. Voltage v(t) volts is applied between A and B and it has got value of +V volts in time interval [0 sec, s sec] and -1.2V volts for all time t > s sec. The current through the circuit is i(t) ampere and voltage drop across the diode is u(t) volts. Plot (i) i(t) vs. t (ii) u(t) vs. t., and (iii) Explain the physics behind these curves. 2+2+3+3

Q.2 (a) Derive the transfer function for the network given in Fig. 2(a). Can this network be used to realize 180° phase shift? 8

 (b) An oscillator circuit is drawn in Fig. 2(b). (i) Identify the frequency selective feedback network and determine its transfer function beta(s). (ii) Derive the expression for the frequency of oscillation. 4+8




2(a)

 

2(b)

**Q. 3** Design a single pole low-pass filter with a gain of 10 in the pass band and 3 dB frequency of 5 kHz. 10

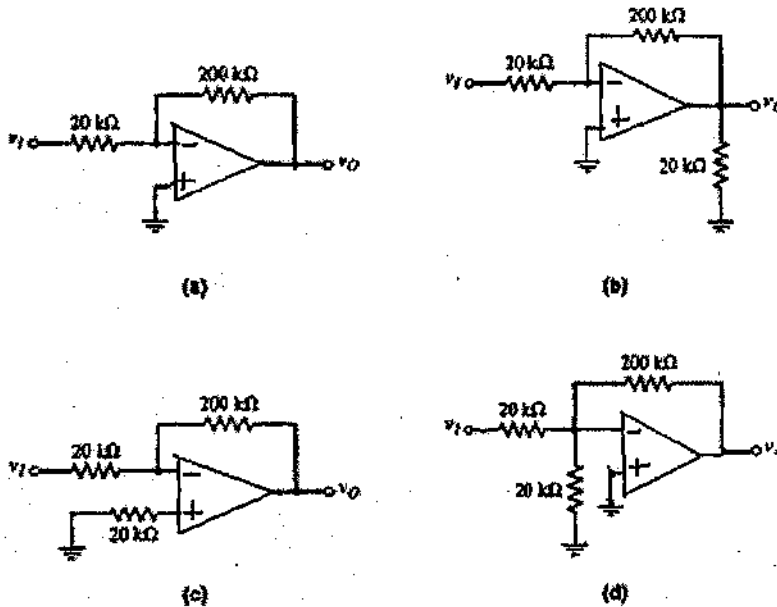**Q. 4** Assuming all the op-amps are ideal, determine the voltage gain and the input resistance of the amplifier configurations given below. 5X4



**Q.5** (a) Draw the combinational logic circuit for the following expressions with AND-OR gates: 4+4

$$Y = \bar{A}\bar{B}C + AB + \bar{A}BC + C$$

$$Y = F(A, B, C, D) = \sum m(1,2,3,6,8,9,10,12)$$

(b) Draw the Karnaugh map for the equation

$$Y = F(A,B,C,D) = \sum m(0,1,2,4,5,6,8,9,10,12,13).$$

Simplify it with the help of the map and draw the simplified logic circuit. 2+4

**Q.6** (a) Draw a 6-input 1-output *multiplexer* with the help of AND, OR and NOT gates. Show the data lines and the related control lines so that only one data line is connected to the output at a time. 4

(b) Develop an edge-triggered J-K flip-flop from a basic R-S flip-flop and show the truth tables. (Hint of various stages: R-S flip flop --- clocked R-S flip flop --- Edge-triggered R-S flip flop --- edge-triggered J-K flip flop). 6

(c) Draw a SERIAL IN – SERIAL OUT 6-bit shift register with the help of 6 D- flip flops. Show the timing diagram for the 6 flip flop outputs Q, R, S, T, U, V when the serial bits 1011 is given at the D input of first flip flop. 6