
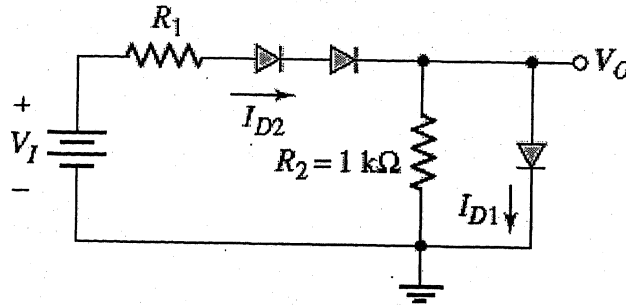


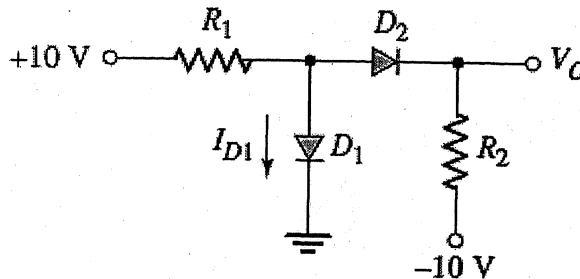1. Assume each diode in the circuit shown in Figure below has a cut-in voltage of $V_\gamma = 0.65\text{V}$. (a) The input voltage is $V_I = 5\text{V}$. Determine the value of R_1 required such that I_{D1} is one-half the value of I_{D2} . What are the values of I_{D1} and I_{D2} ? (b) If $V_I = 8\text{V}$ and $R_1 = 2\text{k}\Omega$, determine I_{D1} and I_{D2} . 10




2. Let $V_\gamma = 0.7\text{V}$ for each diode in the circuit in Figure below (a) Find I_{D1} and V_O for $R_1 = 5\text{k}\Omega$ and $R_2 = 10\text{k}\Omega$. (b) Repeat part (a) for $R_1 = 10\text{k}\Omega$ and $R_2 = 5\text{k}\Omega$. 5+5=10




3. Consider an n-channel enhancement-mode MOSFET with the following parameters: $V_{TN} = 0.75\text{V}$, $W = 40\ \mu\text{m}$, $L = 4\ \mu\text{m}$, $\mu_n = 650\text{ cm}^2/\text{V}\cdot\text{s}$, $t_{ox} = 450\ \text{\AA}$, and $\epsilon_{ox} = (3.9)(8.85 \times 10^{-14})\text{ F/cm}$. Determine the current when $V_{GS} = 2V_{TN}$, for the transistor biased in the saturation region. 10

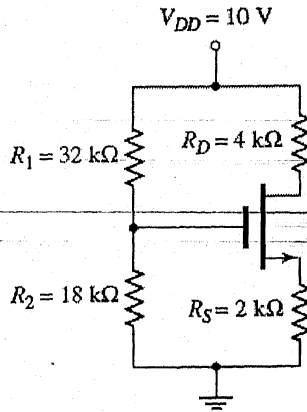
4. In the circuit in Figure below, the transistor parameters are $V_{TN} = 0.8\text{V}$ and $K_n = 0.5\text{ mA/V}^2$. Calculate V_{GS} , I_D , and V_{DS} . 10



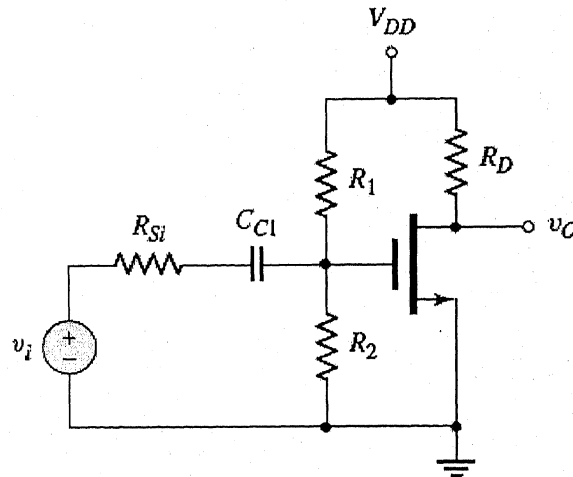5. For the circuit shown in Figure below, the parameters are: $V_{DD} = 10 \text{ V}$, $R_1 = 70 \text{ k}\Omega$, $R_2 = 29.1 \text{ k}\Omega$, and $R_D = 5 \text{ k}\Omega$. The transistor parameters are: $V_{TN} = 1.5 \text{ V}$, $K_n = 0 \text{ mA/V}^2$, and $\lambda = 0.01 \text{ V}^{-1}$. Assume $R_{Si} = 4 \text{ k}\Omega$. Determine the small-signal voltage gain and input and output resistances of a common-source amplifier. 10




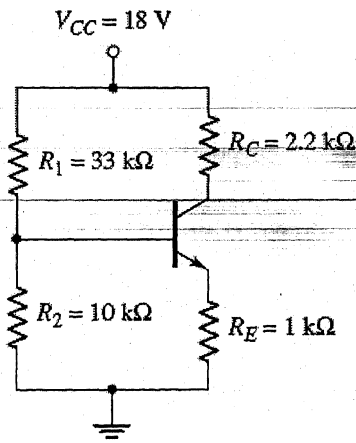6. An NMOS transistor has parameters $V_{TN} = 0.8 \text{ V}$, $k'_n = 80 \mu\text{A/V}^2$, and $\lambda = 0$. (a) Determine the width-to-length ratio (W/L) such that $g_m = 0.5 \text{ mA/V}$ at $I_D = 0.5 \text{ mA}$ when biased in the saturation region. (b) Calculate the required value of V_{GS} . 10
7. a) Calculate the collector and emitter currents, given the base current and current gain. Assume a common-emitter current gain of $\beta = 150$ and a base current of $i_B = 15 \mu\text{A}$. Also assume that the transistor is biased in the forward-active mode.
b) Draw the current components in BJT. And draw the common-emitter mode circuit configuration of BJT 3+5+2=10
8. For the transistor in the circuit shown in Figure below, $\beta = 50$. Determine I_{CQ} and V_{CEQ} . Sketch the load line and plot the Q-point. 10



9. The circuit in Figure below has an op-amp that is ideal except that it has a finite gain A_{od} . (a) If the gain A_{od} is 5×10^3 and the input voltage is $V_I = 3.0V$, what is the output voltage V_O ? (b) If the input voltage is $V_I = 3.0V$ and the output voltage is $V_O = 3.0V$, what is the op-amp gain A_{od} ?

10

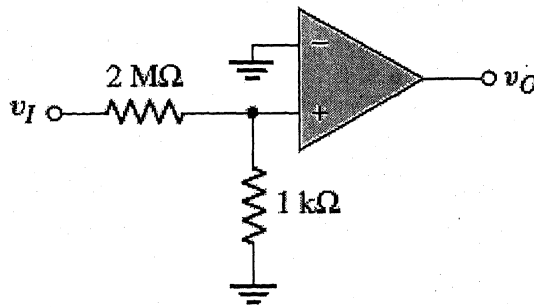

10. Consider the ideal inverting summing amplifier in Figure below. Let $R_1 = 50 \text{ k}\Omega$, $R_2 = 20 \text{ k}\Omega$, $R_3 = 100 \text{ k}\Omega$, and $R_F = 100 \text{ k}\Omega$. (a) Determine V_O if $V_{I1} = 0.5V$, $V_{I2} = 0.75V$, and $V_{I3} = 2.5V$. (b) Determine V_{I3} if $V_{I1} = 1.0V$, $V_{I2} = 0.8V$, and $V_O = -2V$.

10

