


INDIAN INSTITUTE OF TECHNOLOGY

Date: 18th Nov 2011, FN/AN, Time: 3 Hrs., Full Marks: 60, Dept. : CS/EE/EE/IE, No. of Students : 352
 2nd Yr. B.Tech (H), End Autumn Semester, Sub. No.: EC21103, Sub. Name: Introduction to Electronics

Instruction: Answer all questions.

- All waveform sketches / diagrams must be neatly drawn and clearly labeled. Answers must be brief and to the point.
- The final answers (numerical values with unit) should be underlined or enclosed within box.
- For every Question No., start your answer from a new page.
- Avoid writing answers of the various parts of a single question at different locations in your answer-script.
- For any value related to any device parameter or circuit parameter, which you may find not given with a problem, assume suitable value for such parameter.

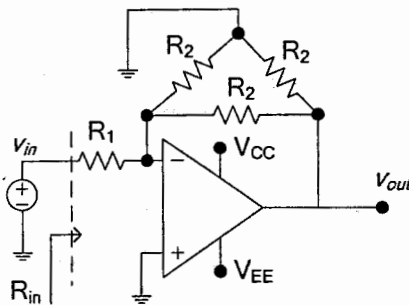Q 1. Problems on OPAMP Circuits and Feedback: 20 Marks



Q 1.A) Given, OPAMP open loop / forward gain ($A_{OL} = \infty$), OPAMP input resistance ($R_{i,op} = \infty$), OPAMP output resistance ($R_{o,op} = 0 \Omega$), $R_2 = 1 \text{ k}\Omega$, $R_1 = 500 \Omega$, $V_{CC} = 5 \text{ V}$, $V_{EE} = -5 \text{ V}$, Saturation voltages are $+4 \text{ V}$ and -4 V .

$$V_{in} = A + B \sin(2\pi \cdot 1 \text{ kHz} \cdot t)$$

Q 1.A.1) Find the value of closed loop voltage gain, V_{out}/V_{in} .

[2]

Q 1.A.2) Find the value of input impedance (R_{in})

[1]


Q 1.A.3) Plot V_{out} and V_{in} if $A = 1 \text{ V}$, $B = 1 \text{ V}$

[1.5]

Q 1.A.4) Plot V_{out} and V_{in} if $A = 1 \text{ V}$, $B = 3 \text{ V}$

[1.5]

Figure 1. OPAMP Circuit (Q 1.A)

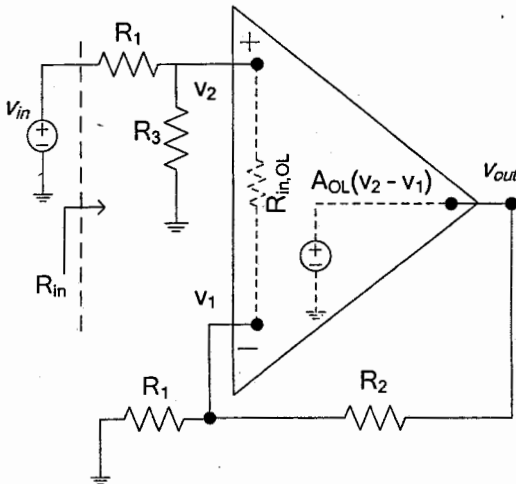

Q 1. B) OPAMP input resistance ($R_{in,OL} = \infty$), $R_2 = 2R_1 = 1 \text{ k}\Omega$.

Q 1. B.1) Find V_{out}/V_{in} expression and value, for OPAMP open loop gain ($A_{OL} = \infty$), $R_3 = \infty$

[1.5]

Q 1. B.2) Find input impedance (R_{in}) for $A_{OL} = \infty$, $R_3 = \infty$

[1]

Q 1. B.3) Find V_{out}/V_{in} expression and value, for $A_{OL} = \infty$, and $R_3 = 1 \text{ k}\Omega$

[1.5]

Q 1. B.4) Find input impedance (R_{in}) for $A_{OL} = \infty$, and $R_3 = 1 \text{ k}\Omega$

[1]

Q 1. B.5) For $A_{OL} = 1000$, $R_3 = 1 \text{ k}\Omega$, find the expression and value of V_{out}/V_{in} .

[2.5]

Q 1. B.6) Identify the type of feedback: What kind of output sampling and what kind of input mixing?

[2]

Q 1. B.7) Find the expression and value of feedback factor (β)?


[2]

Q 1. B.8) For $A_{OL} = 1000$, $R_3 = 1 \text{ k}\Omega$, derive V_{out}/V_{in} using the concept of feedback.

[2]

Figure 2. OPAMP Circuit (Q 1. B)

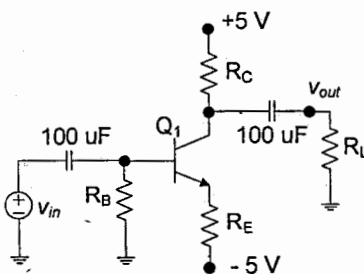Q 2. Problems on Transistor Amplifier and Feedback: 20 Marks



Q 2.A) Consider the amplifier circuit using npn BJT as shown in Figure 3.

$\beta = 100$, $V_A = \infty$, $V_{BE,ON} = 0.7 \text{ V}$, Thermal voltage, $V_{TH} = 26 \text{ mV}$

Circuit parameters: $R_C = R_L = 4.9 \text{ k}\Omega$, $R_B = 419.9 \text{ k}\Omega$, $R_E = 100 \Omega$

Q 2.A.1) Find the values of I_B , V_B , I_C , and V_C .

[2]

Q 2.A.2) Draw the small signal model of the circuit in Figure 3.

[2]

Q 2.A.3) Obtain the expression for A_V and the value.

[2]

Q 2.A.4) Identify the type of feedback i.e. what kind of output sampling and what kind of input mixing.

[2]

Q 2.A.5) Explain why the feedback is a negative feedback?

[1]

Figure 3. BJT Circuit (Q 2.A)

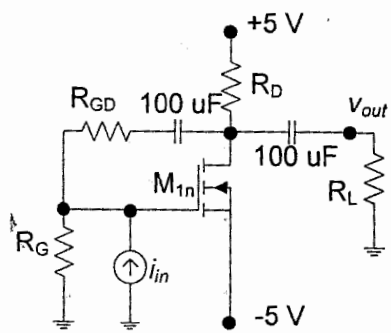


Figure 4. MOSFET Circuit (Q 2.B)

Q 2.B) NMOSFET M_{1n} parameters: $V_{Tn} = 1 \text{ V}$, $\mu_n C_{OX} = 100 \mu\text{A} / \text{V}^2$, $\lambda = 0 \text{ V}^{-1}$, $(W/L) = 2 \mu\text{m} / 1.6 \mu\text{m}$; $R_D = 5 \text{ k}\Omega$, $R_L = 5 \text{ k}\Omega$, $R_G = 100 \text{ k}\Omega$, $R_{GD} = 125 \text{ k}\Omega$

The AC input current, $i_{in} = 100 \cdot \sin(2\pi \cdot 100 \text{ Hz} \cdot t) \text{ mV}$

- Q 2.B.1) Find the values of I_D and V_D . [1]
- Q 2.B.2) Identify the feedback topology i.e. what kind of sampling at output and what kind of mixing at input. [2]
- Q 2.B.3) Draw the small-signal circuit in Figure 4 without feedback. Obtain the expression and value of the open-loop gain, $A_{OL} = v_{out}/i_{in}$ [in V/A]. [1+2]
- Q 2.B.4) Now in the above small signal model put R_{GD} i.e. feedback and find the closed loop gain $A_{CL} = v_{out}/i_{in}$ [in V/A]. [2]
- Q 2.B.5) From the above closed loop gain A_{CL} identify the expression and value of feedback factor (β). [2]

Q 3. Problems on Digital Electronics: 20 Marks

- Q 3.A.1) Find the decimal equivalent of the binary number $(01011011)_2$. [1]
- Q 3.A.2) Find the 8-bit binary equivalent (2's complement form) of the decimal number $(-125)_{10}$. [1]
- Q 3.A.3) What is the 8-bit result of $(00100001)_2 + (00011001)_2$? (Both the numbers are in 2's complement form) [1]
- Q 3.A.4) What is the 8-bit result of $(00010111)_2 - (01010101)_2$? (Both the numbers are in 2's complement form) [1]

Q 3.B) Assuming both the normal input (e.g. A) and the complement input (e.g. A') are available, implement the following logic functions:

- Q 3.B.1) $F_1 = A + B' D' + C D'$ using only NAND gates. You may use NAND gates more than 2 inputs, if required. [2]
- Q 3.B.2) $F_2 = A' B' + C' D' + B' C'$ using only NOR gates. You may use NOR gates more than 2 inputs, if required. [2]

AB →	00	01	11	10
CD ↓				
00	1			1
01				
11				
10	1			X

Figure 5. Karnaugh Map (Q 3.C.1)

- Q 3.C.1) What is the logic function in the simplest form for the Karnaugh Map shown in Figure 5? [2]
- Q 3.C.2) Write down the truth table for the logic function, $Y_1 = A'B'C' + AB'C'D' + A'B'C + ACD' + ABC'D + A'CD' + AB'CD'$. [1]
From the truth table, draw the Karnaugh Map and then find the simplest form of the logic function for Y_1 . [2]
- Q 3.C.3) Repeat the question in (Q 3.C.2) with the additional condition that, for the input value-combinations of $(A, B, C, D) = (1, 1, 0, 0)$, and $(0, 1, 0, 1)$, the logic output of Y_1 is "Don't Care". Show the new truth-table and find the simplest form of the modified Y_1 using a new Karnaugh Map. [1]
[2]

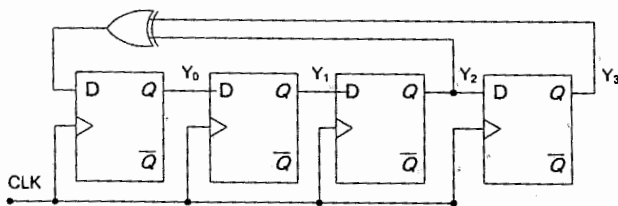


Figure 6. Digital Logic Circuit (Q 3.D)

For the circuit in Figure 6 plot CLK, Y_0 , Y_1 , Y_2 , and Y_3 from 0 ms to 4.5 ms. All D-FF's are positive edge-triggered.

Q 3.D) At time $t = 0 \text{ ms}$, assume $Y_0 = Y_1 = Y_2 = '0'$, $Y_3 = '1'$ [4]

